

①

22.02.2021

CS223

-Digital Design-


Section: 2

Name : Barin Saday


ID: 21902967

Lab: 2

Schematic for 1-bit full adder:

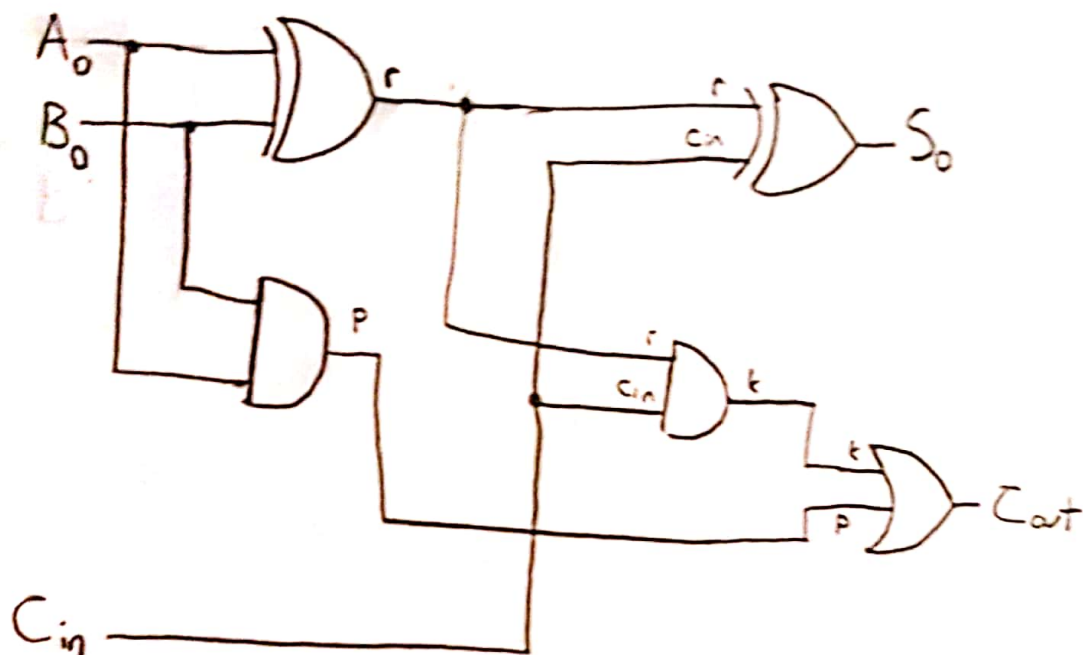

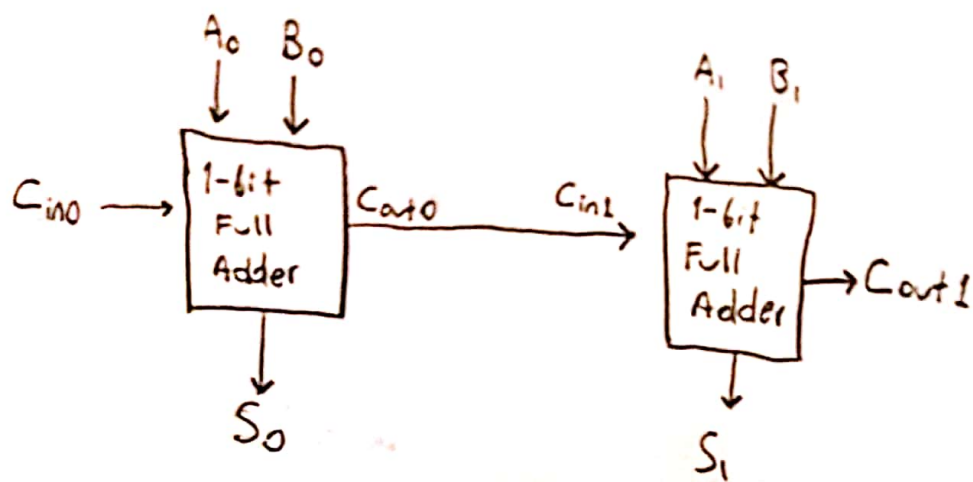Schematic for 2-bit full adder: (using 1-bit full adders)



Note: $C_{out0} = C_{in1}$

One-Bit Full Adder Dataflow:

```
module one_bit_full_adder (  
    input logic A, B, Cin,  
    output logic S,Cout  
);  
  
    //local logic variables  
    logic r, p, k;  
    assign r = A ^ B;  
    assign p = A & B;  
    assign k = r & Cin;  
  
    //assigning output logics  
    assign S = r ^ Cin;  
    assign Cout = k | p;  
Endmodule
```

Structural One-Bit Full Adder:

```
module st_one_bit_full_adder(  
    input A,  
    input B,  
    input Cin,  
    output S,  
    output Cout  
);  
  
    wire r, p, k;  
  
    xor u1(r, A, B);  
    and u2(p, A, B);  
    and u3(k, r, Cin);
```

```
xor u4(S, r, Cin);  
or u5(Cout, k, p);  
Endmodule
```

Test Bench One-Bit Full Adder:

```
module tb_one_bit_full_adder();
```

```
    logic A, B, Cin, S, Cout;
```

```
    st_one_bit_full_adder uut(
```

```
        .A(A),
```

```
        .B(B),
```

```
        .Cin(Cin),
```

```
        .S(S),
```

```
        .Cout(Cout)
```

```
    );
```

```
    initial
```

```
    begin
```

```
        A = 0;
```

```
        B = 0;
```

```
        Cin = 0;
```

```
        #10;//1
```

```
        A = 1;
```

```
        B = 0;
```

```
        Cin = 0;
```

```
        #10;//2
```

```
        A = 0;
```

```
        B = 1;
```

Cin = 0;

#10;//3

A = 1;

B = 1;

Cin = 0;

#10;//4

A = 0;

B = 0;

Cin = 1;

#10;//5

A = 1;

B = 0;

Cin = 1;

#10;//6

A = 0;

B = 1;

Cin = 1;

#10;//7

A = 1;

B = 1;

Cin = 1;

#10;//8

end

endmodule

Structural Two-Bit Adder:

```
module st_two_bit_adder(  
    input A0,  
    input A1,  
    input B0,  
    input B1,  
    input Cin,  
    output S0,  
    output S1,  
    output Cout  
);  
  
    // c is Cout of first adder and Cin of second adder  
    wire c;  
    st_one_bit_full_adder g1(A0, B0, Cin, S0, c); //found S0 and c  
  
    st_one_bit_full_adder g2(A1, B1, c, S1, Cout ); //found S1 and Cout  
Endmodule
```

TestBench Two-Bit Adder:

```
module tb_two_bit_adder();  
  
    logic A0, A1, B0, B1, Cin, S0, S1, Cout;  
  
    st_two_bit_adder f(  
        .A(A), .B(B), .Cin(Cin),  
        .S0(S0), .S1(S1), .Cout(Cout)  
    );  
endmodule
```

initial

begin

A0 = 0;

B0 = 0;

A1 = 0;

B1 = 0;

#10;

A0 = 1;

B0 = 0;

A1 = 0;

B1 = 0;

#10;

A0 = 0;

B0 = 1;

A1 = 0;

B1 = 0;

#10;

A0 = 1;

B0 = 1;

A1 = 0;

B1 = 0;

#10;

A0 = 0;

B0 = 0;

A1 = 1;

B1 = 0;

#10;

A0 = 1;

B0 = 0;

A1 = 1;

B1 = 0;

#10;

A0 = 0;

B0 = 1;

A1 = 1;

B1 = 0;

#10;

A0 = 1;

B0 = 1;

A1 = 1;

B1 = 0;

#10;

A0 = 0;

B0 = 0;

A1 = 0;

B1 = 1;

#10;

A0 = 1;

B0 = 0;

A1 = 0;

B1 = 1;

#10;

A0 = 0;

B0 = 1;

A1 = 0;

B1 = 1;

#10;

A0 = 1;

B0 = 1;

A1 = 0;

B1 = 1;

#10;

A0 = 0;

B0 = 0;

A1 = 1;

B1 = 1;

#10;

A0 = 1;

B0 = 0;

A1 = 1;

B1 = 1;

#10;

A0 = 0;

B0 = 1;

A1 = 1;

B1 = 1;

#10;

```
A0 = 1;
```

```
B0 = 1;
```

```
A1 = 1;
```

```
B1 = 1;
```

```
#10;
```

```
end
```

```
always
```

```
begin
```

```
    Cin = 0;#5;
```

```
    Cin = 1;#5;
```

```
end
```

```
endmodule
```